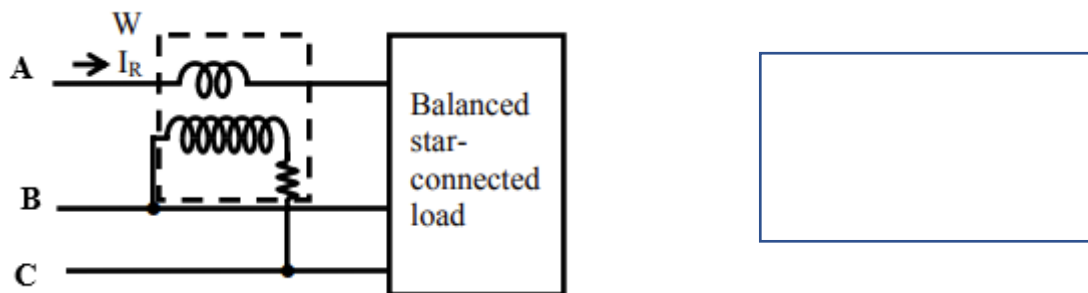


Q3

Name:

Class Serial Number:

1. Calculate the readings of the wattmeter (W) connected as shown in Fig. The load is a balanced star-connected one, with impedance of $(2+j14) \Omega$ per phase, fed from a three-phase, 400 V, balanced supply, with the phase sequence as ABC. [5]



2. Find the Thevenin's equivalent voltage across the terminals a, b if $X = 9$. Also the maximum power transferred to Z_L . [10]

