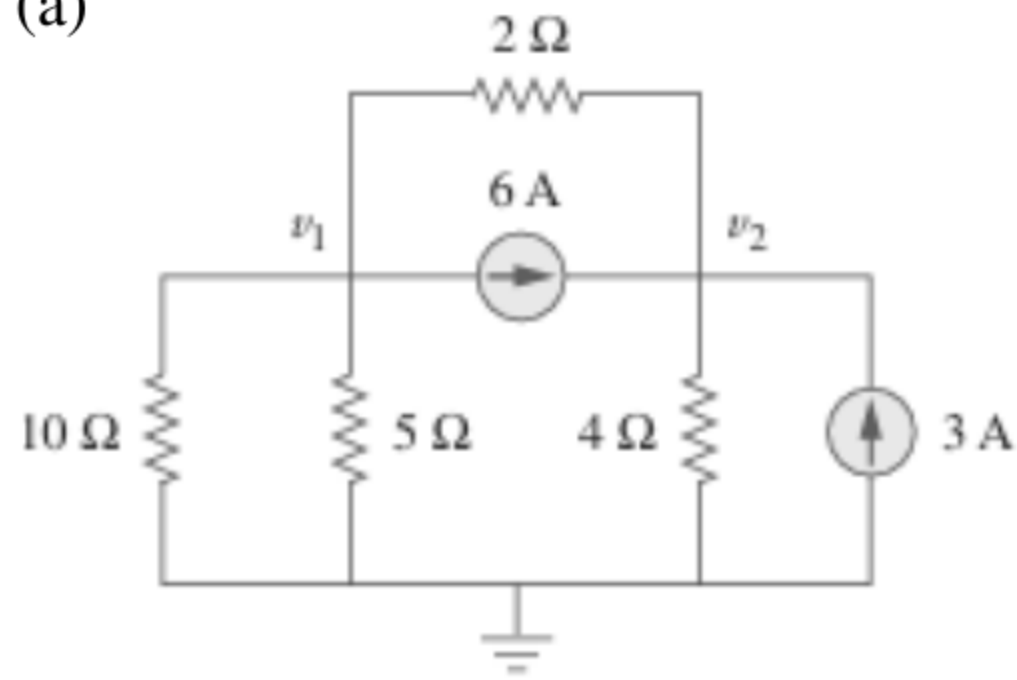



Tutorial-1

- Find the node voltages v_1 and v_2 using nodal analysis.

(a)



(b)

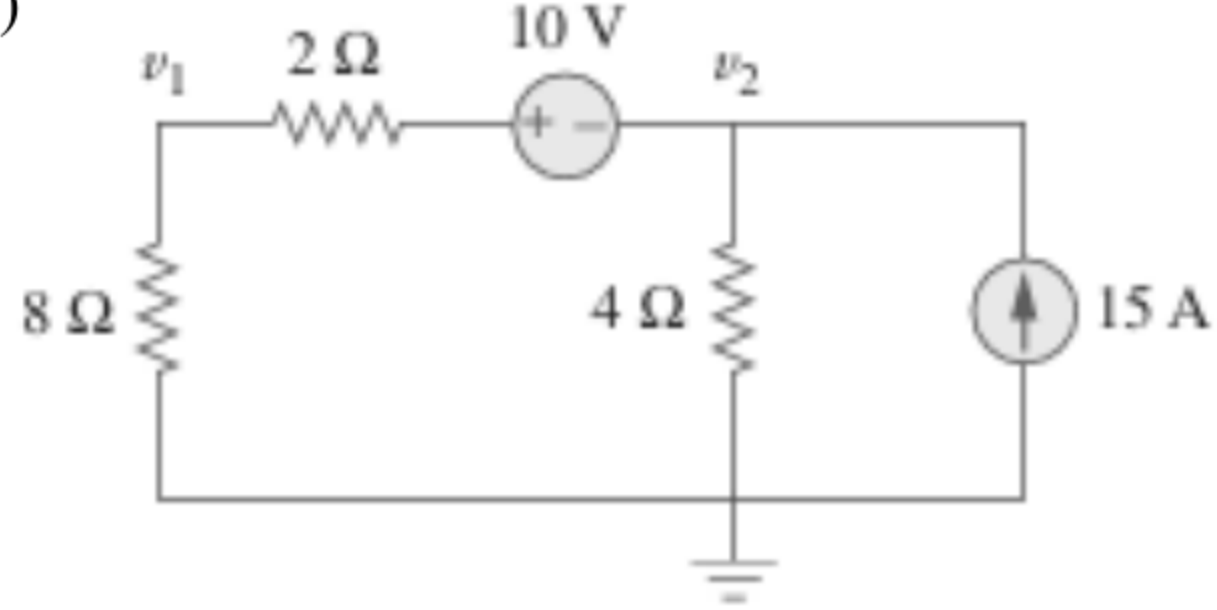

- Apply nodal analysis to solve for V_x in Fig. 3 and V_o in Fig. 4.

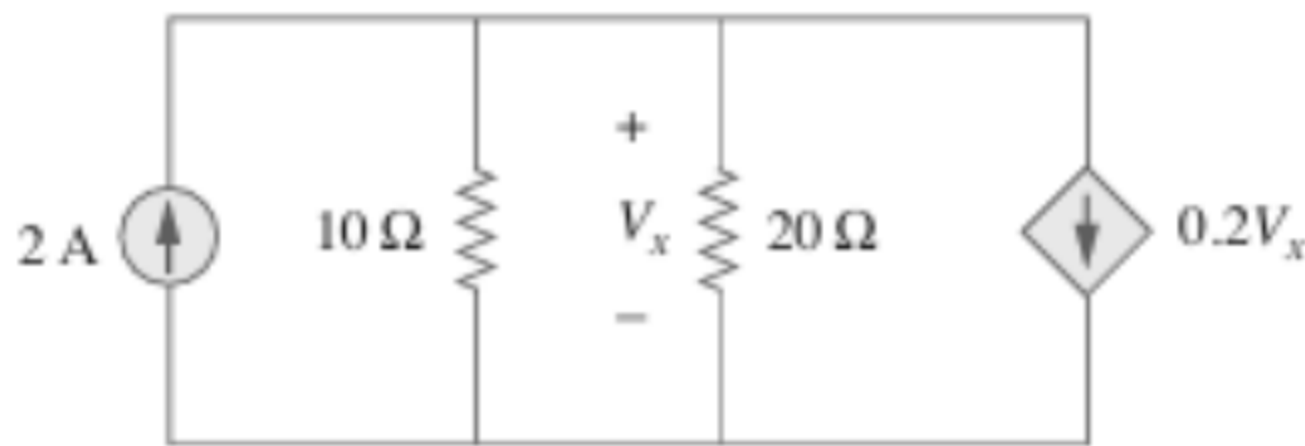


Fig. 3

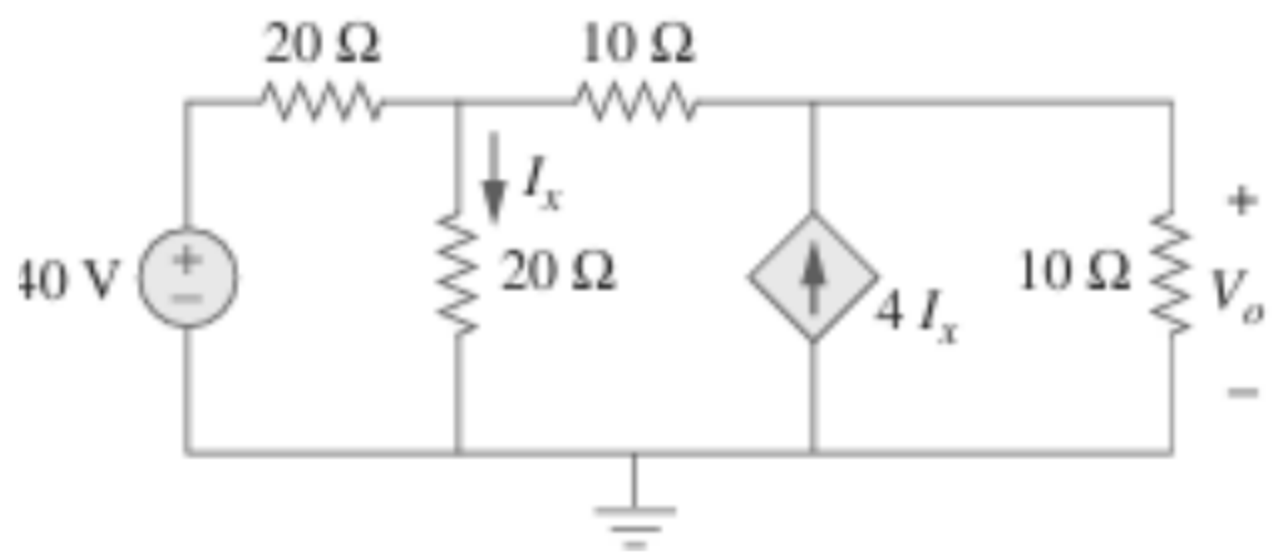


Fig. 4

- Find the node voltages v_1 , v_2 , v_3 using nodal analysis (Fig. 5)

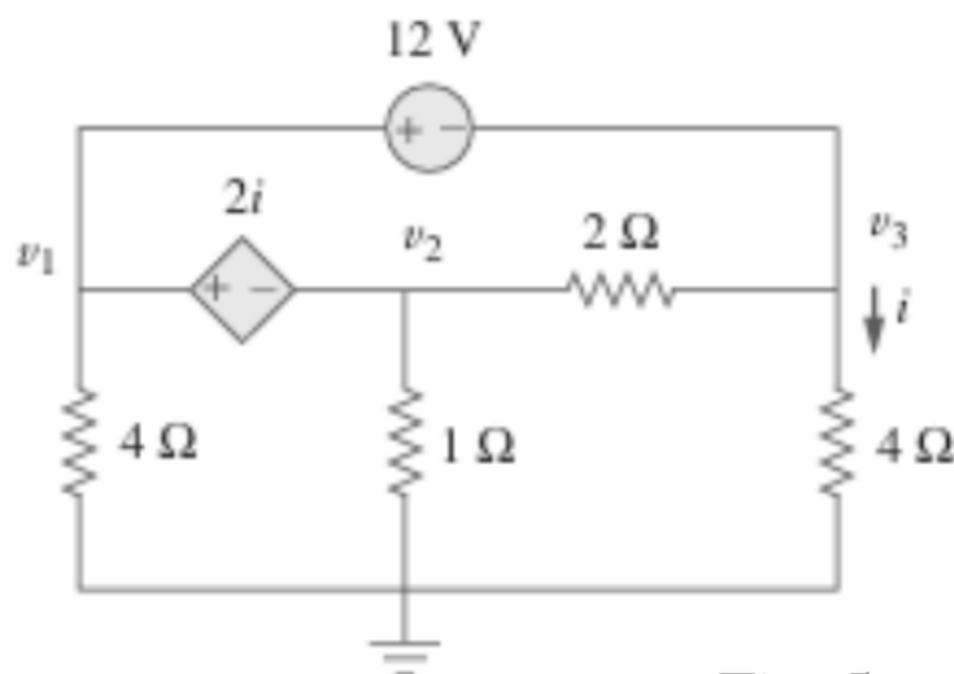


Fig. 5

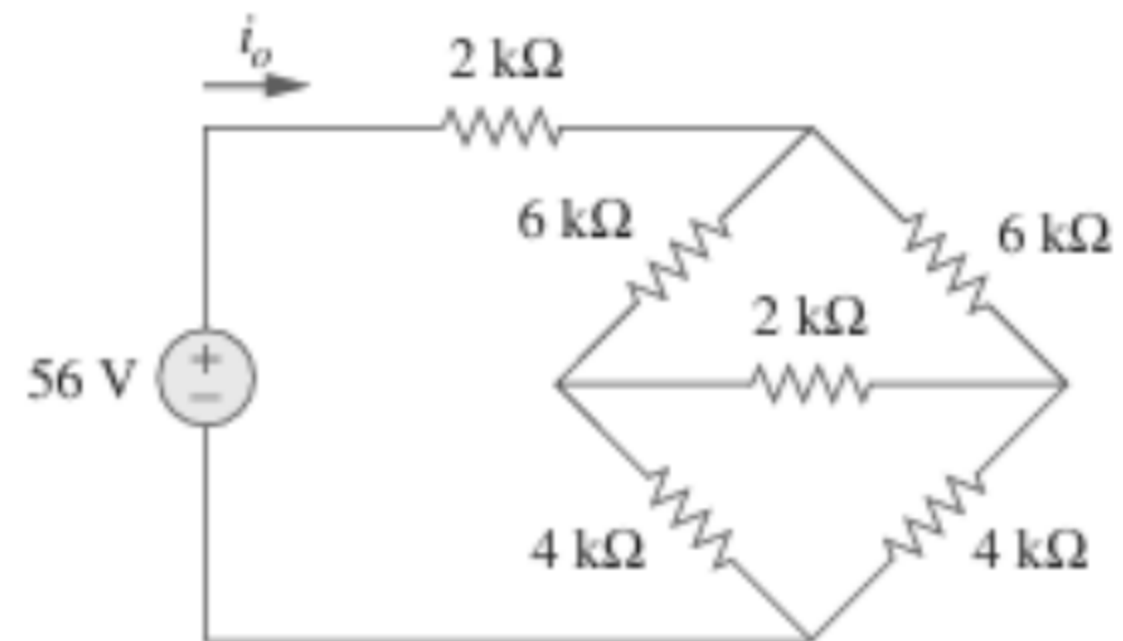


Fig. 6

- In Fig.6, find i_o using mesh analysis.

- Find the mesh currents i_1 and i_2 (Fig.7).

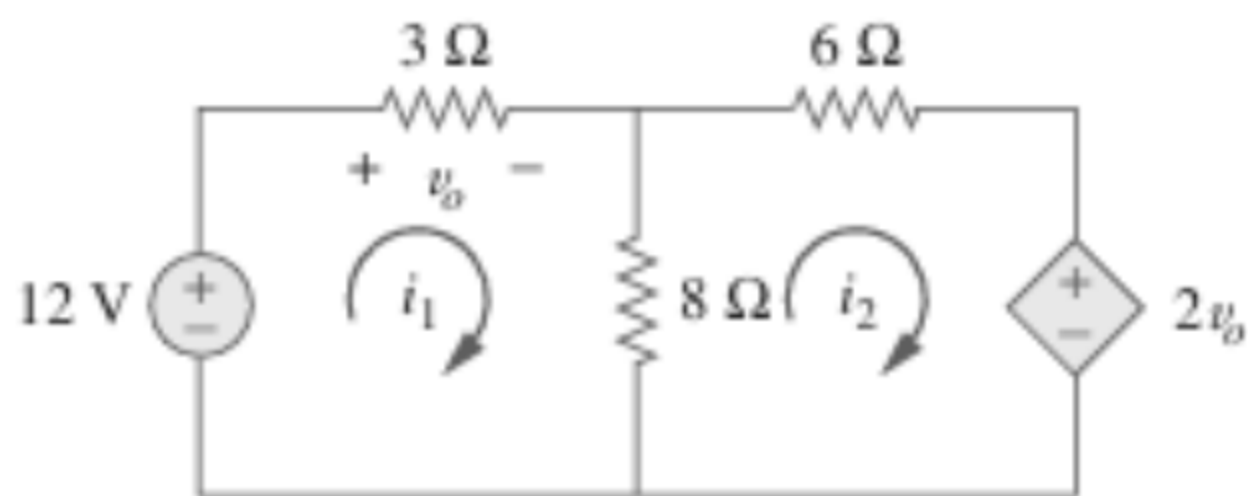


Fig.7

- Obtain v_o and i_o using mesh analysis (Fig.8).


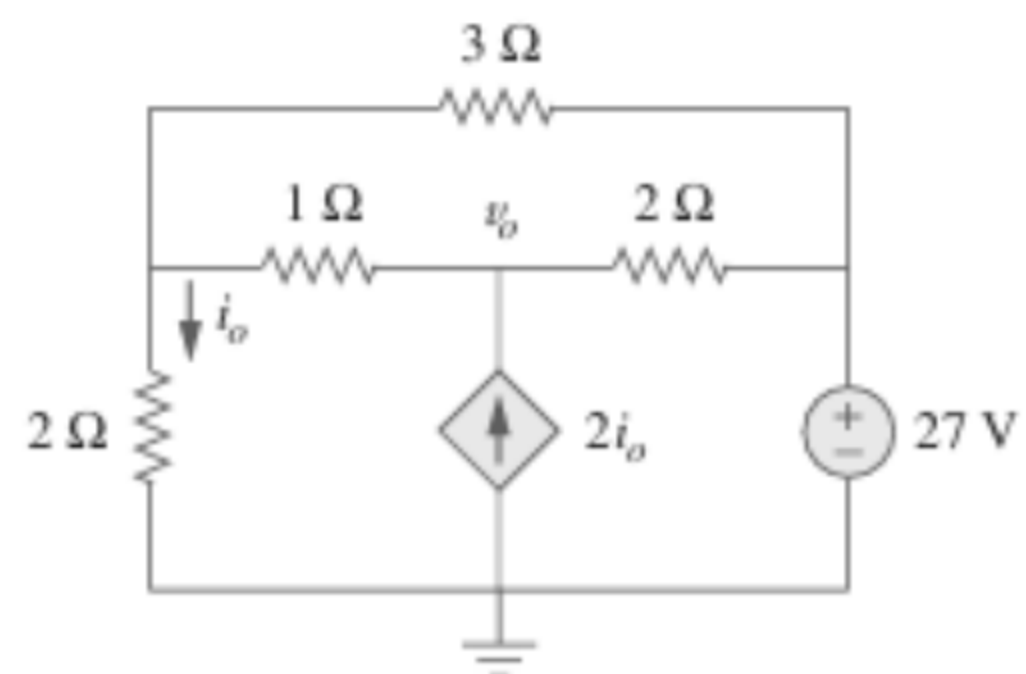


Fig. 8

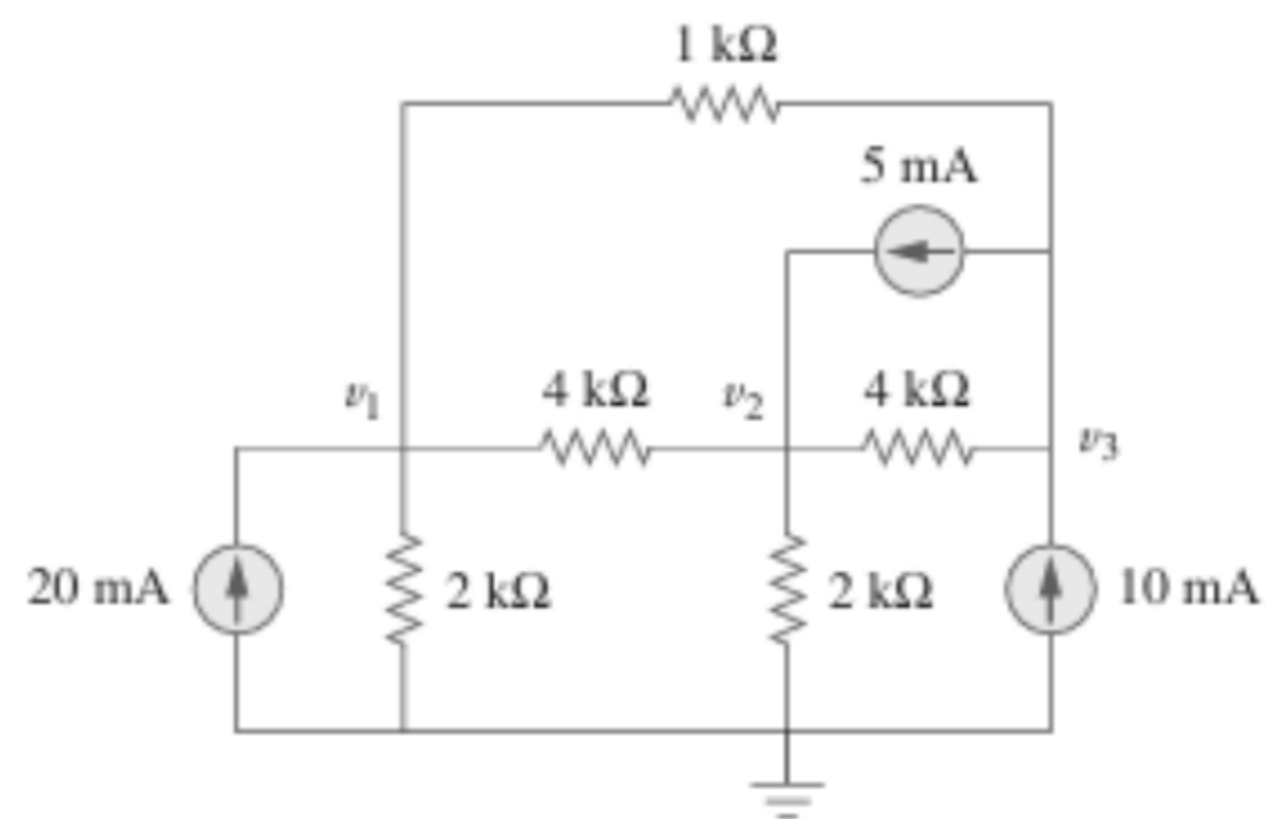7. Write the nodal equations by inspection.



8. Write the mesh equations by inspection.

